2020 Digital IC Design Training

LAB4: Adaptive Threshold Engine

1. Introduction

Threshold is the simplest method of image segmentation. From a grayscale image, threshold can be used to create binary images

Please design an Adaptive Threshold Engine (ATE). As shown in Fig 1, the function of the ATE circuit is used to separate a grayscale image from the foreground image. The system block diagram is shown in Fig 2. Its detailed specifications will be described later. Each input and output signal refers to **Table 1**.



Fig 1. The function of Adaptive Threshold Engine

2. Design Specifications

2.1 Block Overview

 


Fig 2. Block Overview

2.2 I/O Interface

Table 1. I/O Interface

Signal Name	I/O	Width	Description	
clk	I	1	clock for the computational system	
reset	I	1	reset the state of the computational system	
			when it asserts	
pix_data	I	8	the 8-bit input pixel data	
bin	О	1	each pixel data is converted to 1-bit data by	
			threshold	
threshold	О	8	threshold data for single region	

2.3 System Description

2.3.1 Image input

The size of input image is 48X32 (6X4 block). Each block has 8X8 points. The image input order is sequentially, as shown in the block number sequence of Fig 3.

When performing Threshold processing, it takes the block-base as a unit. The leftmost and rightmost lines do not need to be processed, so their bin and threshold are all outputs 0. As shown in Fig 3, blocks 0, 6, 12, 18 and The 5, 11, 17, 23 blocks do not need to be processed.

 


Fig 3. Input image block

2.3.2 Adaptive Threshold

The purpose of threshold is to distinguish the foreground and background of a grayscale image. For each point of the image block, if it is greater than or equal to the threshold value of the block, it outputs 1 and vice versa. The Adaptive threshold indicates that this threshold is calculated.

The threshold calculation method for this ATE circuit uses the average of the maximum and minimum values in a single 8x8 block, i.e. threshold=(Max+Min)/2, and if the threshold is a floating point number, the unconditional carry is taken.

For each point:

bin=1 if pix_data >= threshold
bin=0 if pix_data < threshold</pre>

In Fig 4, for example, the maximum value of the block is 192, and the minimum value is 48. Then the threshold = (192+48)/2=120, so the output is the right picture.

 


Fig 4. Single block threshold

2.4 Timing Diagram

2.4.1 Output Order

The test circuit will be reset at the beginning. After the reset is completed, the entire image content will be input in an uninterrupted manner. The order of the input blocks is from left to right, from top to bottom. In a single block, the value of each point

is also from left to right and from top to bottom. The order of output is the same as the order of input, but the output will add an output delay time one block later than the input, and the output will be uninterrupted.

As shown in Fig 5, the output delay is set to 1 cycle. When the test circuit inputs the content of the first block, the ATE sends the calculation result of the first block at the next cycle.

 


Fig 5. Output order

2.4.2 Output timing

The input and output timing specifications of this circuit are as follows:

 


Fig 6. Timing definition

Table 2

Symbol	Description	Value
Tcycle	Clock cycle	User definition

T _{IS}	Setup time	1/2 clock cycle
$T_{ m IH}$	Hold time	1/2 clock cycle
Tos	Setup time	1/2 clock cycle
Тон	Hold time	1/2 clock cycle

3. Scoring

3.1 Functional Simulation (pre-sim)

All of the result should be generated correctly, and you will get the following message in ModelSim simulation. You can turn off the timing check in pre-sim only.

4. Report file

You have to describe how the circuit is designed as detailed as possible, and the flow summary result and simulation results are necessary.